 


Radiation Hardness Test Chip



Schaltungstechnik
und Simulation

Matthias Harter, Peter Fischer

Uni Mannheim

Overview


1. Reminder: Radiation Damage & Remedies
2. Chip description
3. First results

Note: Not yet clear how much rad. hardness we need for CBM... This little work is just a contribution to discussions...






Radiation Damage – very superficial

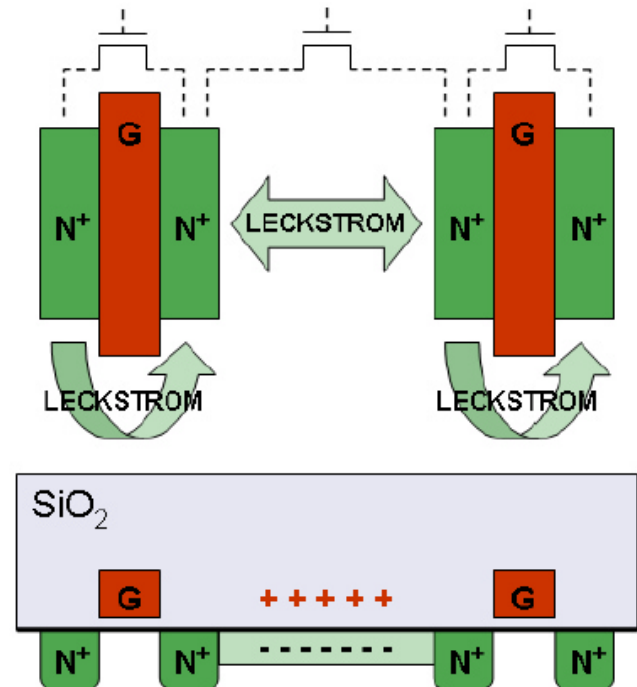- Ionizing radiation leads to positive charges in thick oxides
 - ⇒ Threshold voltage shift – decreasing for NMOS
 - ⇒ leakage 'around' NMOS
 - ⇒ creation of parasitic NMOS (field oxide)
 - PMOS remains unaffected.
- Large local charge deposition can lead to
 - SET: single event transient = spike on signal
 - SEU: single event upset = bit flip
 - SEGR: single event gate rupture (really?)




Remedies

- Enclosed NMOS (other shapes are possible!)
 - Guard rings between NMOS with drains on different potential
 - Special FF design / redundancy / voting / hamming... for SEU / SET
-
- Consequences:
 - need special extraction files
 - larger area (x4 for digital designs)
 - larger caps -> often more power in digital (x4)
 - Hard to make good NMOS current source (large L no possible)
 - Hard to make good NMOS switches (very asymmetric & large caps)

 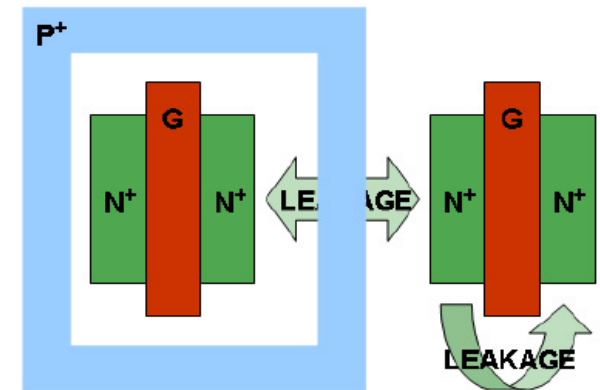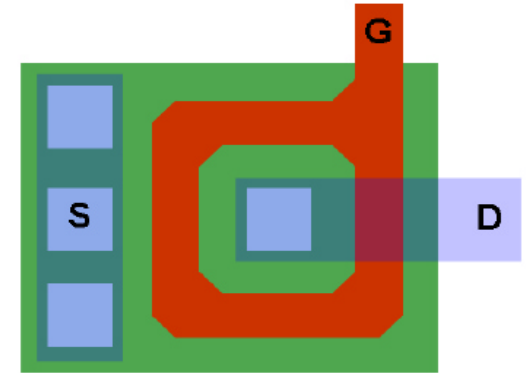

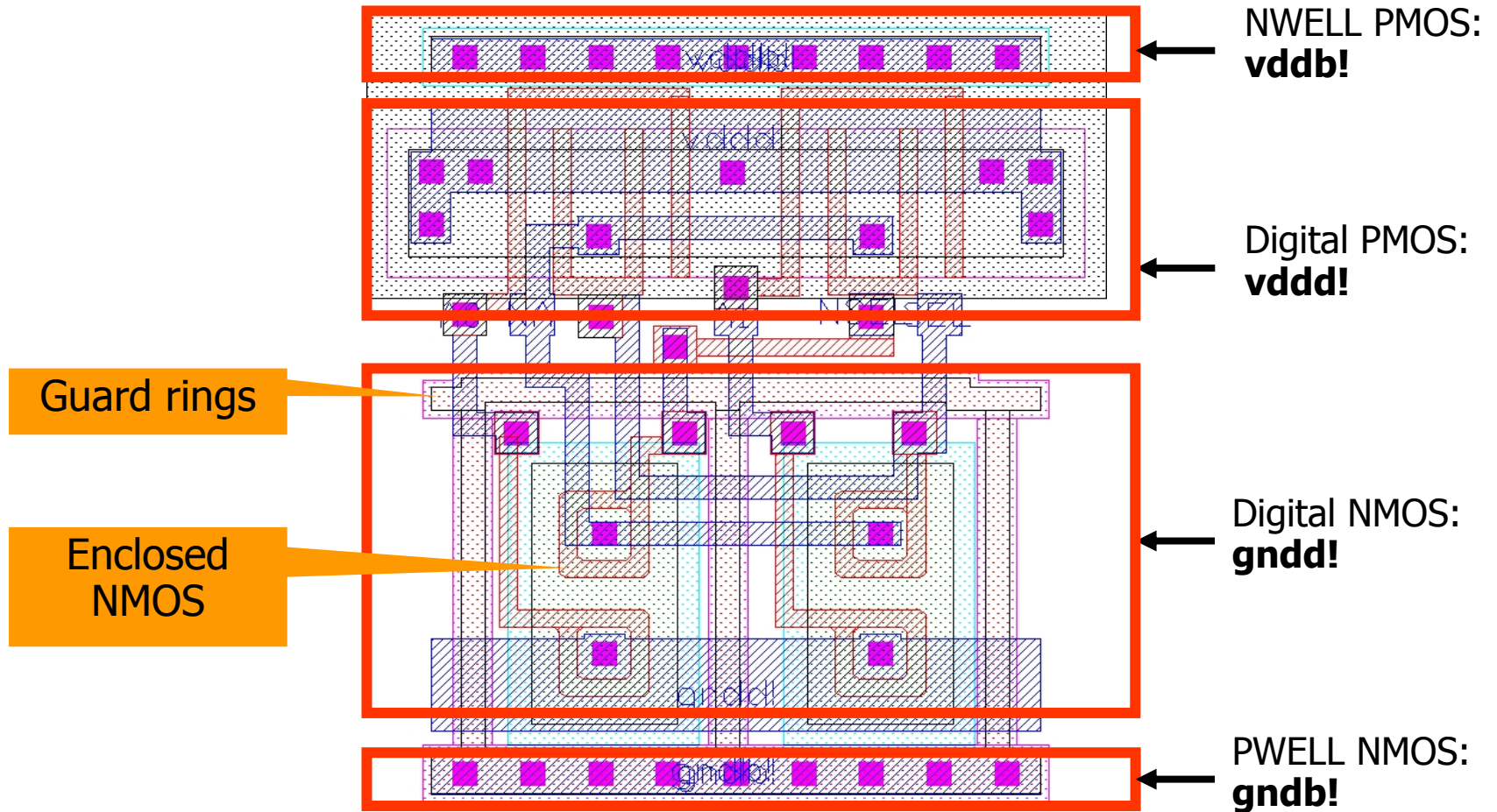
Example: radhard MUX2->1

- Our 'mixed mode' lib uses separate nets for digital wells (nwell, pwell)




Radhard vs. Normal Layout

 - We want to compare both types.
Therefore made cells with equal transistor / layout size:



Hard

 

Normal


Test Chip

Goals:

- Verify models (speed)
- Measure SEU during irradiation
- Measure leakage after irradiation for 'hard' and 'non-hard' layouts
- Keep chip very simple for easy testing with minimal equipment


Circuits:

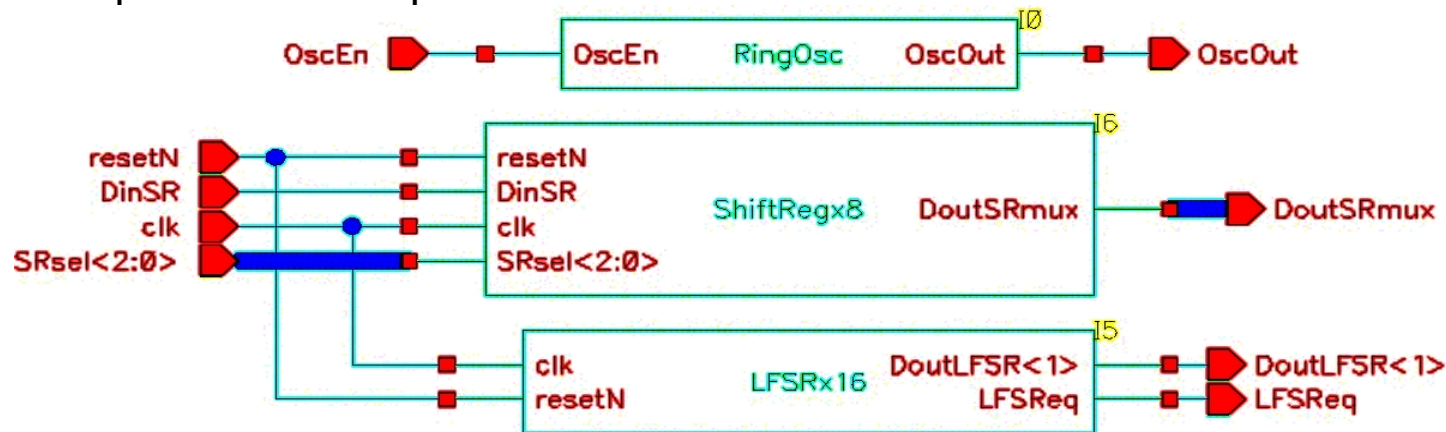- 1 **ring oscillator** with 101 inverters & enable. Sim. frequency: 176 MHz
- 8 normal **shift registers**, 16 Bit, common data input, one output via 8-1 MUX
- 16 linear feedback shift registers (**LFSR**) producing pseudo random bit sequences, 16 bit long. Test **equality** of all 16 LFSRs to detect SEU.
- Rad hard output drivers.
- All pads have ESD protection diodes




Radhard vs. Normal Layout

 - Chip is implemented twice:
 1. radhard with round NMOS + guard rings
 2. Normal Layout. Widths of MOS are same as for round devices
- Identical pinout!
- 17 pins per side (just one side of a JLCC68)
- Switch between the two versions by rotating carrier in socket!



Test Chip Layout



This chip

 


could cut here



Another project..

 
 


Detail of pinout...

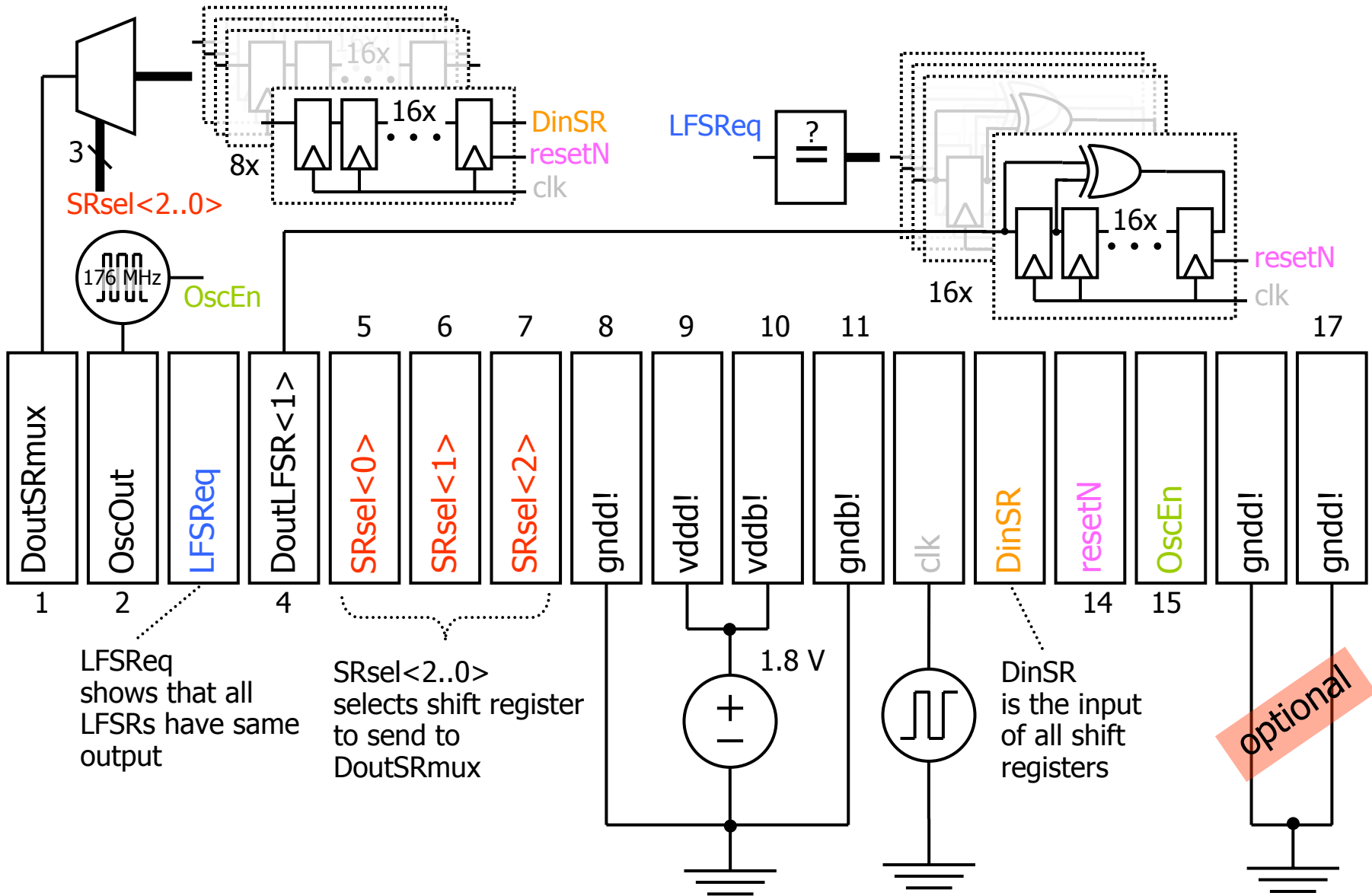



Measurements: Ring Oscillator

 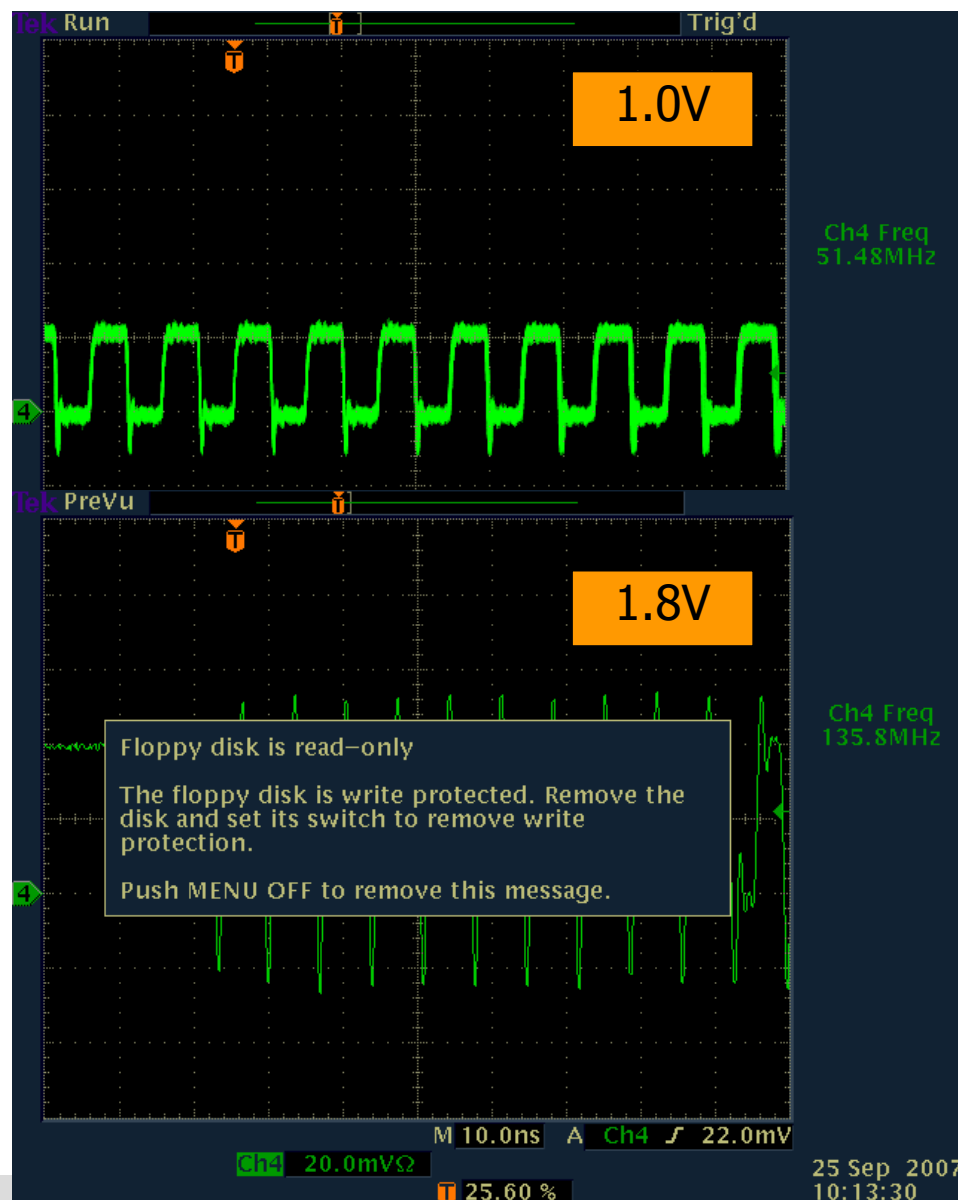- Works as expected.
- Simulated speed: 176MHz
- Measured:
 - Supply [V] Speed [MHz]
 - 1.8 150
 - 1.7 140
 - 1.6 130
 - 1.5 117
 - 1.2 78
 - 1.0 51



Measurements: LFSR

 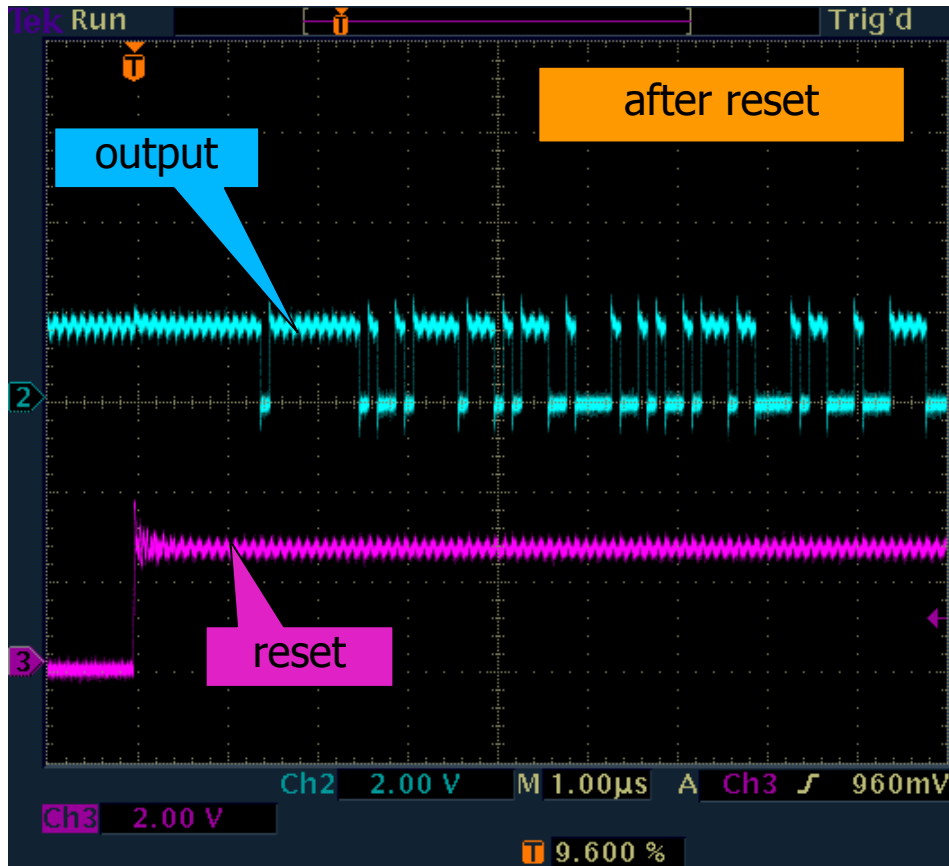- Works as expected
- Produces nice spectrum on Analyzer...



Problems & Summary

- Shift registers also work as expected
- Problem: Large supply current. May be setup but more likely wrong type of substrate connection somewhere...
- Good agreement in speed. Must check voltage dependence.
- Next steps:
 - Decide if irradiation of this is interesting
 - May resubmit in 3 weeks if there is a bug. May increase register length.

